

Exercise 1.

Using the truth table, prove the following equalities.



$$a + \bar{a} \cdot b = a + b, \quad a \oplus b = \bar{a} \cdot b + a \cdot \bar{b}, \quad \overline{a \oplus b} = a \cdot b + \bar{a} \cdot \bar{b}.$$

Exercise 2.

1. How would you hardware-implement a four-input OR gate using only two-input OR gates ?
2. How would you hardware-implement a four-input AND gate using only two-input AND gates ?
3. How do you implement three-input EX-OR logic functions with the help of two-input EX-OR gates ?
4. How can you implement a NOT circuit using a two-input EX-OR gates ?
5. How do you implement a three-input EX-NOR function using only two-input EX-NOR gates ?

Exercise 3.

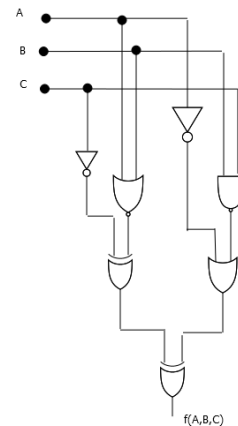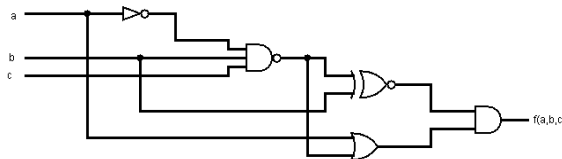1. Give the output-logical function expressions of the figures bellow




2. Give the truth table of each boolean function.

Exercise 4.

Let us define a circuit by the following logical function

$$F(A, B, C) = \overline{A \oplus B} + C.$$

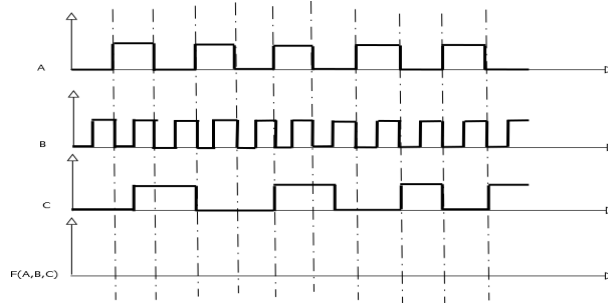1. Give the graphic representation of the circuit.
2. Describe the output waveform for the input signals given in the figure bellow.



3. Give the corresponding truth table

Exercise 5. 1. Find the dual of $a \cdot b \cdot c \cdot \bar{d} + a \cdot \bar{b} \cdot \bar{c} \cdot d + \bar{a} \cdot \bar{b} \cdot \bar{c} \cdot \bar{d}$.

2. Find the complement of $a + [(b + \bar{c}) \cdot d + \bar{e}] \cdot f$.

Exercise 6. Simplify the following Boolean expressions.

1. $S = \bar{a} \cdot b \cdot (a + \bar{b} + c)$.
2. $S = \bar{a} \cdot \bar{b} \cdot \bar{c} \cdot \bar{d} + a \cdot \bar{b} \cdot \bar{c} \cdot \bar{d} + a \cdot b \cdot \bar{c} \cdot \bar{d} + a \cdot b \cdot \bar{c} \cdot \bar{d}$.
3. $S = a + b \cdot \bar{c} + \bar{a} \cdot (\overline{b \cdot \bar{c}}) \cdot (a \cdot d + b)$.
4. $S = (a \oplus b) \cdot b + a \cdot b$.

Exercise 7.

Let us define a circuit by the truth table bellow.

1. Give the logical expression of the output Y .
 - In the form of sum of products.
 - In the form of product of sums
2. Simplify the two expressions using the theorems of Boolean algebra.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Exercise 8.

Let us consider the following logic functions

$$f(a, b, c, d) = a.b + \bar{a}.\bar{c}.\bar{d} \text{ and } g(a, b, c, d) = (\bar{a} + \bar{b} + \bar{c}).(a + d).$$

- Give a logic circuit based on 2-input NAND gates and a logic circuit based on 2-input NOR gates for each of these functions.

Exercise 9.

We define a logical function f by the following truth table.

1. Write the disjunctif canonical form of the output.
2. Using theorems and laws of Boolean algebra to simplify the logical expression.
3. Give a logic circuit, using only 2-input NAND gates to implement the function f .

a	b	c	$f(a, b, c)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Exercise 10. Let f be a boolean function defined by the truth table bellow.

1. Represent f by his disjunctive canonical form. (First canonical form)
2. Use the Karnaugh mapping method to obtain the simplified expression of f .
3. Implement the logical function f , using only 2-input NAND gates.

x	y	z	$f(x, y, z)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Exercise 11.

Let us give the boolean function defined by

$$f(a, b, c) = \prod(1, 4, 6)$$

1. Write function's expression as product of sums and sum of products.
2. Let us define the Boolean function g by $g(a, b, c) = a.b + \bar{c}$.
— Write minterm and maxterm expressions of f .
3. Simplify the Boolean functions f and g using the Karnaugh mapping method
4. Using the Karnaugh mapping method, simplify the Boolean function h , defined by $h(a, b, c, d) = \Sigma(0, 3, 4, 6, 7, 8, 9, 10, 12, 14, 15) + \Sigma_{\varphi}(1, 2, 5, 11, 13, 15)$.

Exercise 12.

		ab			
		00	01	11	10
c	0	1	1	1	1
c	1	1	0	0	1

		ab			
		00	01	11	10
c	0	1	x	1	x
c	1	1	0	1	1

		ab			
		00	01	11	10
cd	00	1	0	0	1
cd	01	0	0	0	0
cd	11	1	1	1	1
cd	10	1	1	1	1

		<i>ab</i>			
		<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>
<i>cd</i>	<i>00</i>	0	1	1	0
	<i>01</i>	0	0	0	0
	<i>11</i>	1	0	0	1
	<i>10</i>	1	1	1	1

		<i>ab</i>			
		<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>
<i>cd</i>	<i>00</i>	1	1	0	1
	<i>01</i>	0	0	<i>x</i>	0
	<i>11</i>	1	<i>x</i>	0	1
	<i>10</i>	1	1	<i>x</i>	1

		<i>ab</i>			
		<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>
<i>cd</i>	<i>00</i>	<i>x</i>	0	0	1
	<i>01</i>	1	0	0	1
	<i>11</i>	<i>x</i>	0	0	0
	<i>10</i>	1	1	<i>x</i>	1